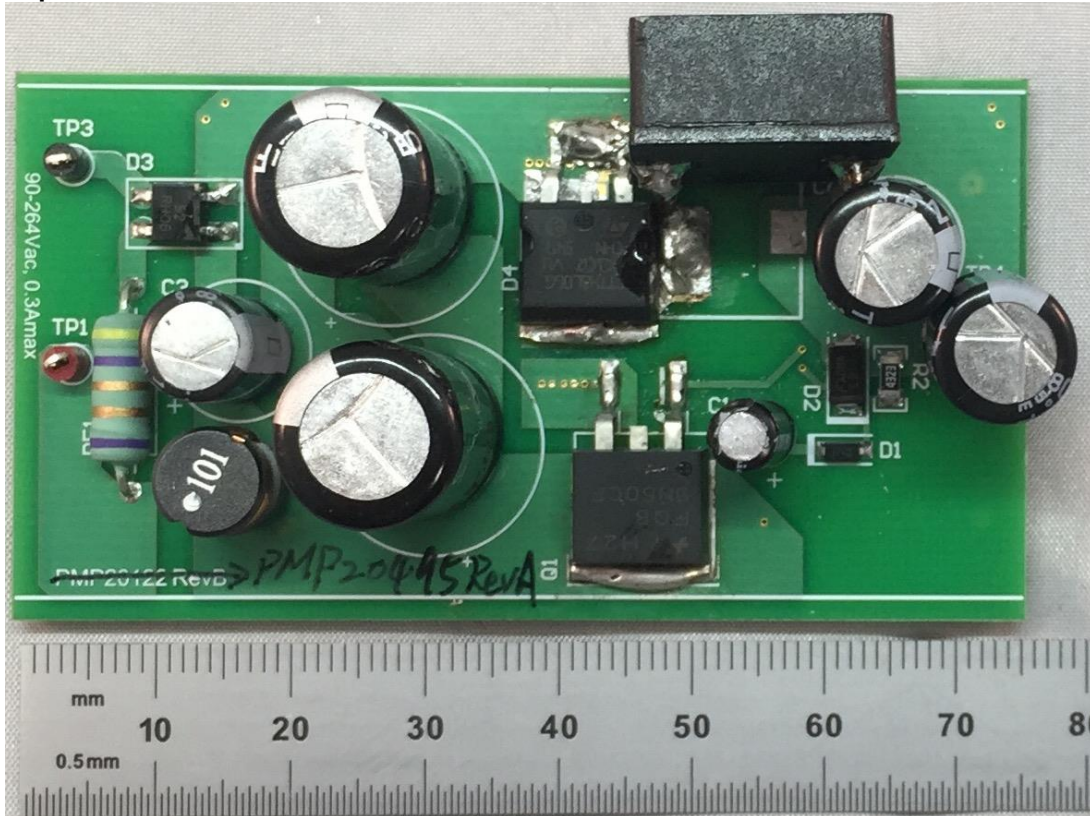



## 1 Photo

The photographs below show the PMP20495 Rev A assembly. PMP20495 Rev A circuit was built on PMP20122 Rev B PCB.

### Top side




### Bottom side

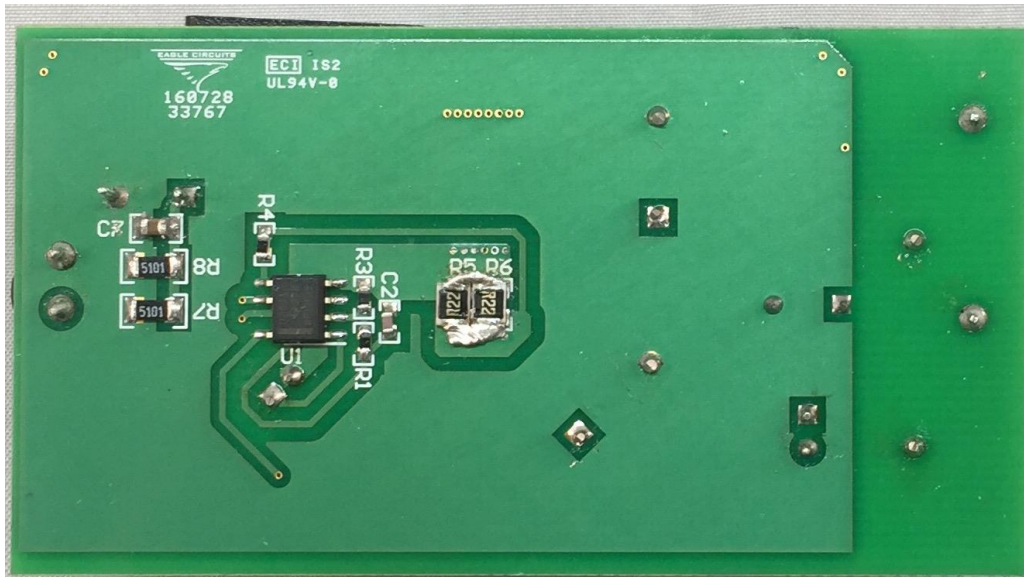
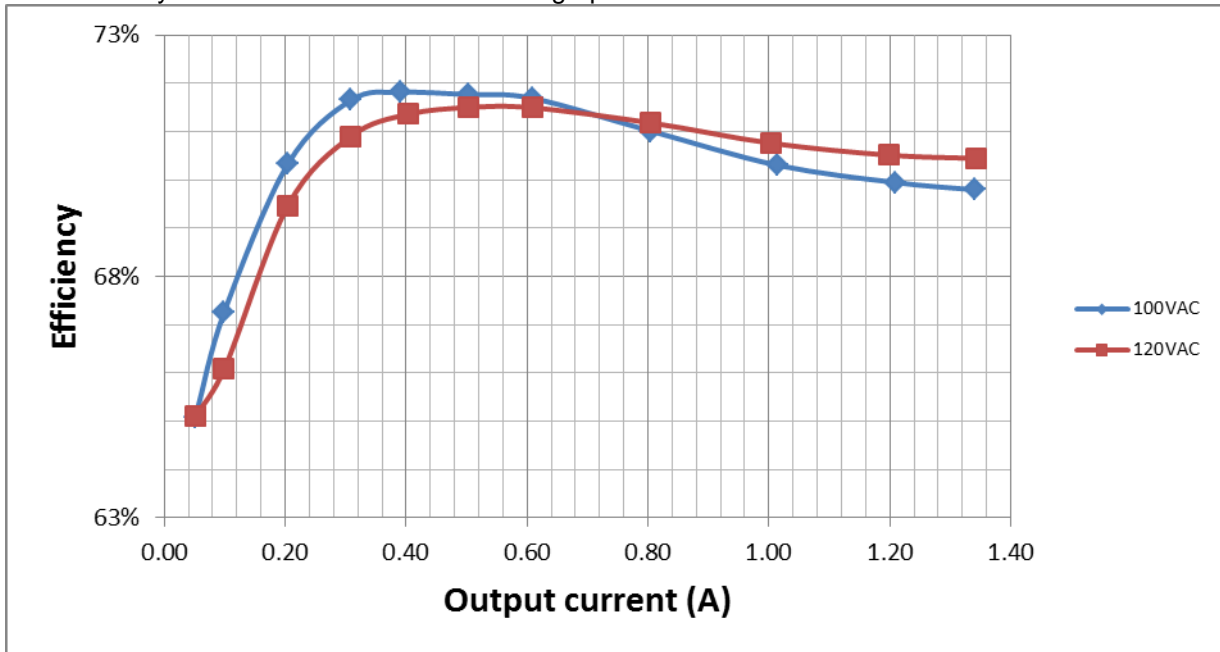
## 2 Converter Efficiency

The efficiency data is shown in the tables and graph below.



### V<sub>in</sub>=100V<sub>AC</sub>/60Hz

V <sub>in</sub> (V)	I <sub>in</sub> (mA)	P.F.	P <sub>in</sub> (W)	V <sub>out</sub> (V)	I <sub>out</sub> (A)	P <sub>out</sub> (W)	Losses(W)	Efficiency (%)
100.05	0.37	0.61	22.79	11.87	1.34	15.91	6.88	69.79%
100.08	0.34	0.61	20.50	11.86	1.21	14.34	6.16	69.95%
100.16	0.29	0.59	17.11	11.86	1.01	12.03	5.08	70.30%
100.05	0.23	0.57	13.45	11.86	0.81	9.55	3.90	71.01%
100.13	0.18	0.55	10.08	11.86	0.61	7.22	2.85	71.69%
99.96	0.16	0.54	8.33	11.86	0.50	5.98	2.35	71.77%
100.12	0.12	0.52	6.46	11.87	0.39	4.64	1.82	71.81%
100.15	0.10	0.50	5.12	11.87	0.31	3.67	1.45	71.65%
100.18	0.07	0.47	3.45	11.90	0.20	2.43	1.02	70.32%
100.01	0.04	0.43	1.76	11.95	0.10	1.18	0.58	67.26%
100.03	0.02	0.40	0.93	11.84	0.05	0.60	0.32	65.07%
100.05	0.00	0.31	0.08	11.97	0.00	0.00	0.08	0.00%

### V<sub>in</sub>=120V<sub>AC</sub>/50Hz


V <sub>in</sub> (V)	I <sub>in</sub> (mA)	P.F.	P <sub>in</sub> (W)	V <sub>out</sub> (V)	I <sub>out</sub> (A)	P <sub>out</sub> (W)	Losses(W)	Efficiency (%)
120.05	0.32	0.59	22.63	11.87	1.34	15.94	6.69	70.44%
120.10	0.29	0.58	20.15	11.86	1.20	14.21	5.94	70.51%
120.05	0.25	0.56	16.81	11.86	1.00	11.90	4.92	70.76%
120.03	0.20	0.55	13.41	11.86	0.81	9.55	3.87	71.18%
119.98	0.16	0.53	10.09	11.85	0.61	7.22	2.88	71.49%
120.02	0.14	0.51	8.35	11.85	0.50	5.97	2.38	71.50%
120.05	0.11	0.50	6.70	11.86	0.40	4.78	1.92	71.36%
120.11	0.09	0.48	5.17	11.87	0.31	3.67	1.51	70.90%
120.14	0.06	0.45	3.49	11.89	0.20	2.43	1.07	69.46%
120.08	0.04	0.41	1.79	11.94	0.10	1.18	0.61	66.07%
120.09	0.02	0.38	0.94	11.83	0.05	0.62	0.33	65.11%
120.12	0.00	0.30	0.08	11.96	0.00	0.00	0.08	0.00%

### 3 Thermal Images

The thermal images below show board thermal images under 12V/1.34A output condition. The ambient temperature was 25°C with no forced air flow. The output was at 12V/1.34A.

$V_{in}=100V_{AC}/60Hz$


Top view

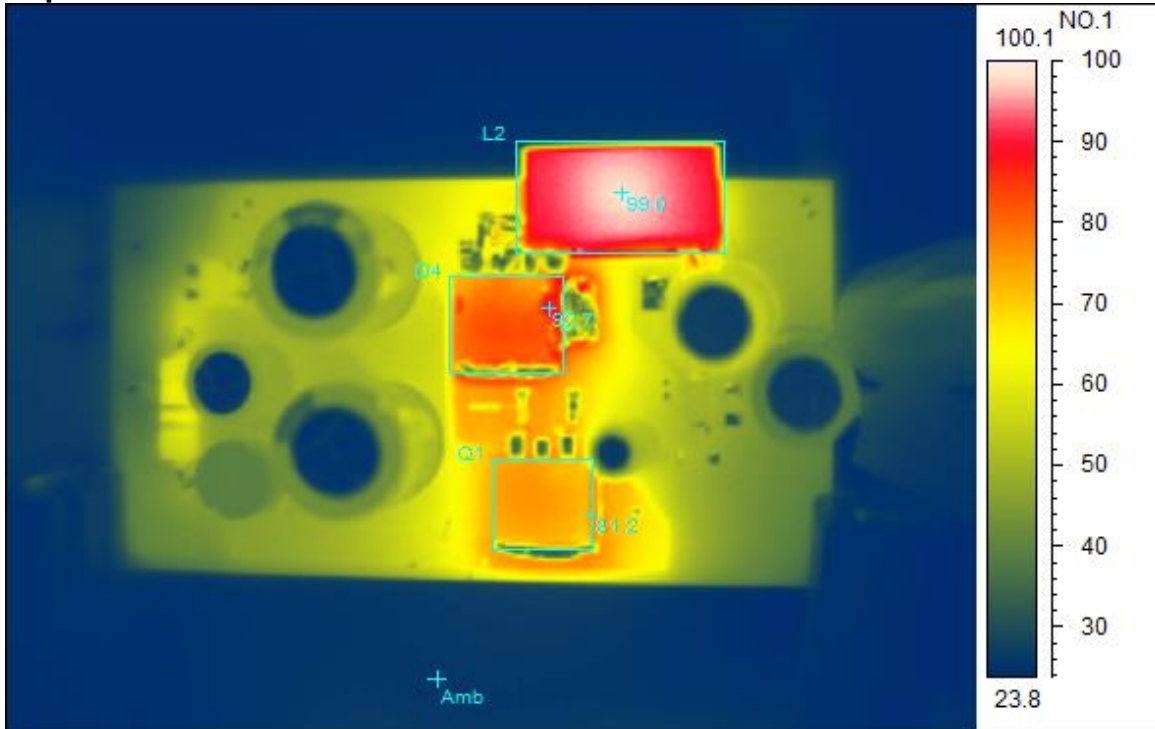

Spot analysis	Value
Amb Temperature	26.6°C
Area analysis	Value
L2Max	99.0°C
D4Max	92.7°C
Q1Max	81.2°C

**V<sub>in</sub>=100V<sub>AC</sub>/60Hz**


**Side view**

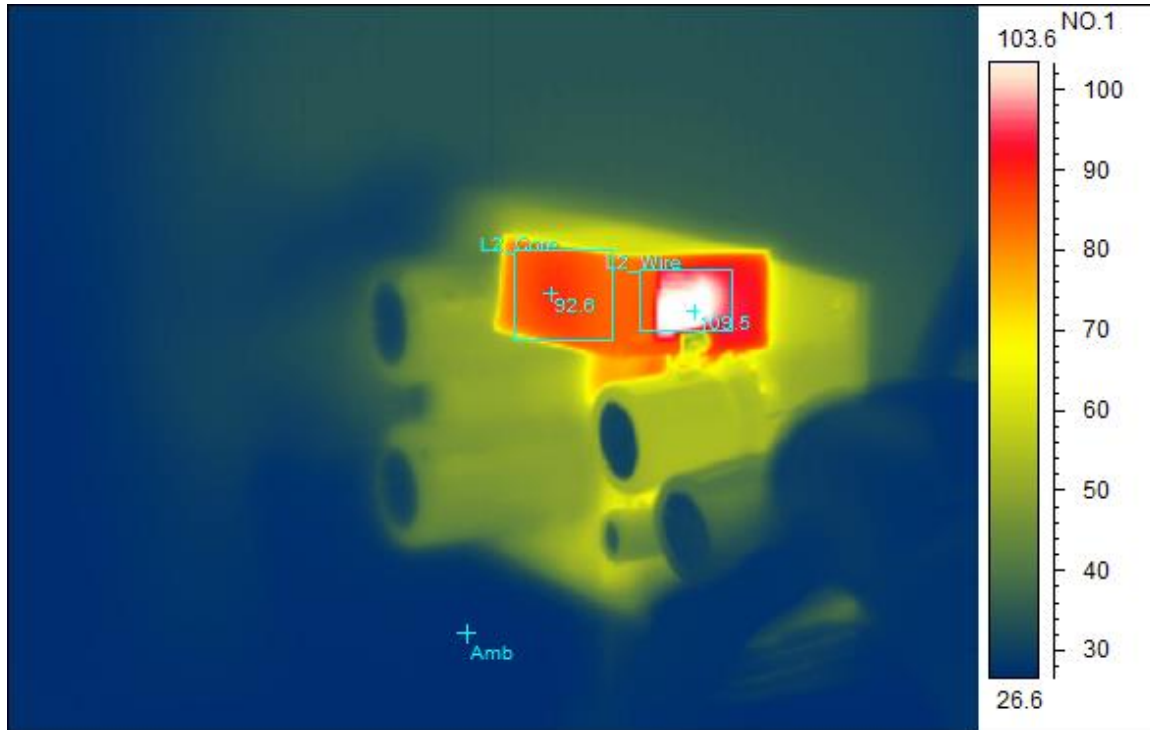

Spot analysis	Value
Amb Temperature	27.0°C
Area analysis	Value
L2_CoreMax	92.6°C
L2_WireMax	109.5°C

**$V_{in}=100V_{AC}/60Hz$**


**Bottom view**

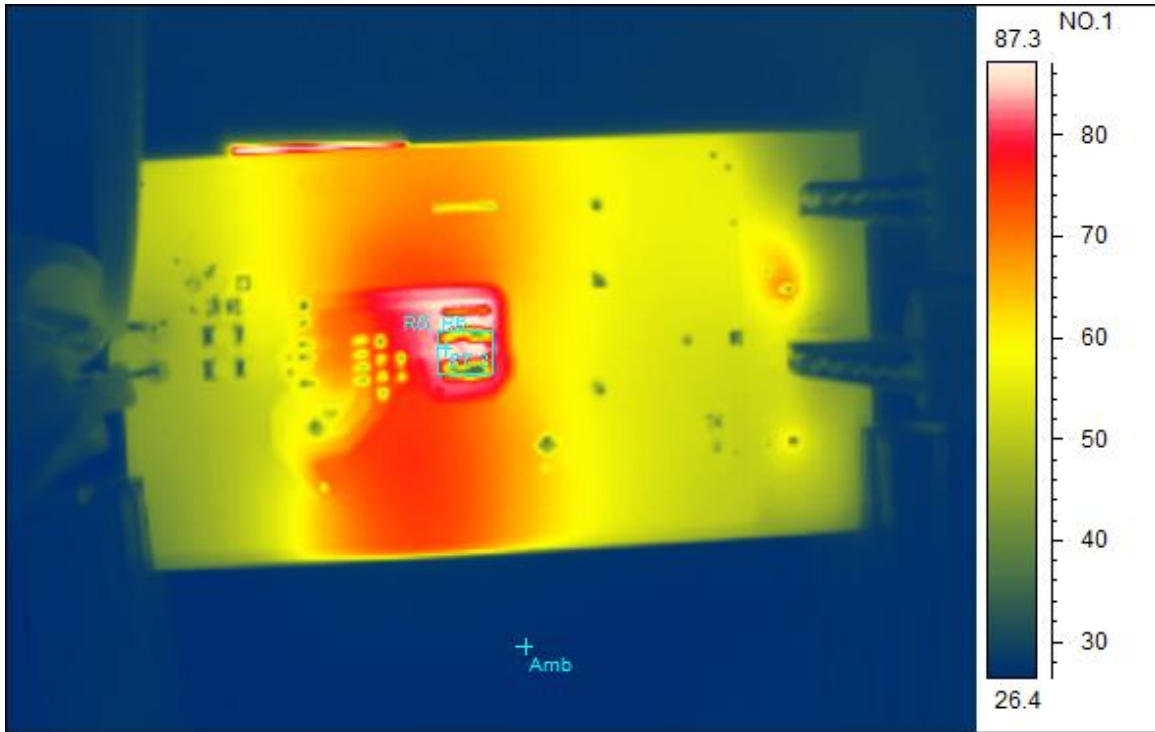

Spot analysis	Value
Amb Temperature	27.1°C
Area analysis	Value
R5, R6Max	87.3°C

$V_{in}=120V_{AC}/60Hz$

Top view

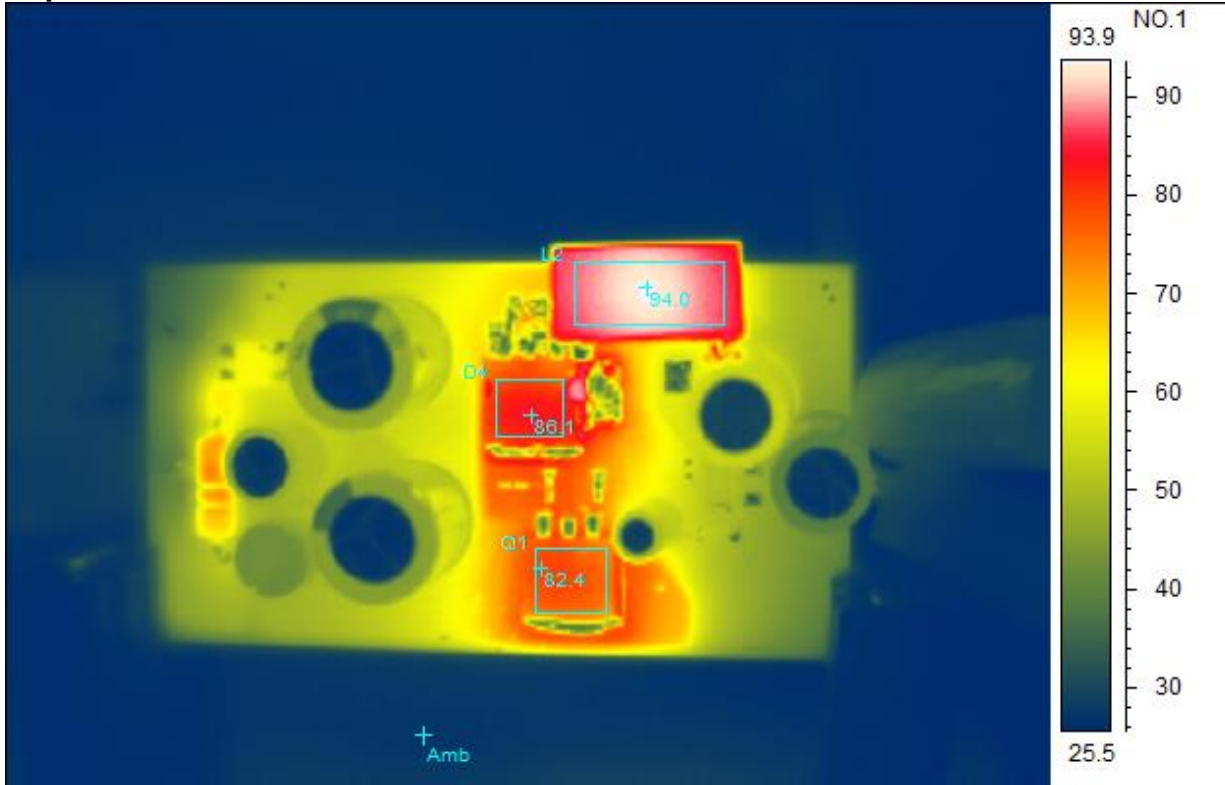


Spot analysis	Value
Amb Temperature	27.6°C
Area analysis	Value
L2Max	94.0°C
D4Max	86.1°C
Q1Max	82.4°C



$V_{in}=120V_{AC}/60Hz$


Side view

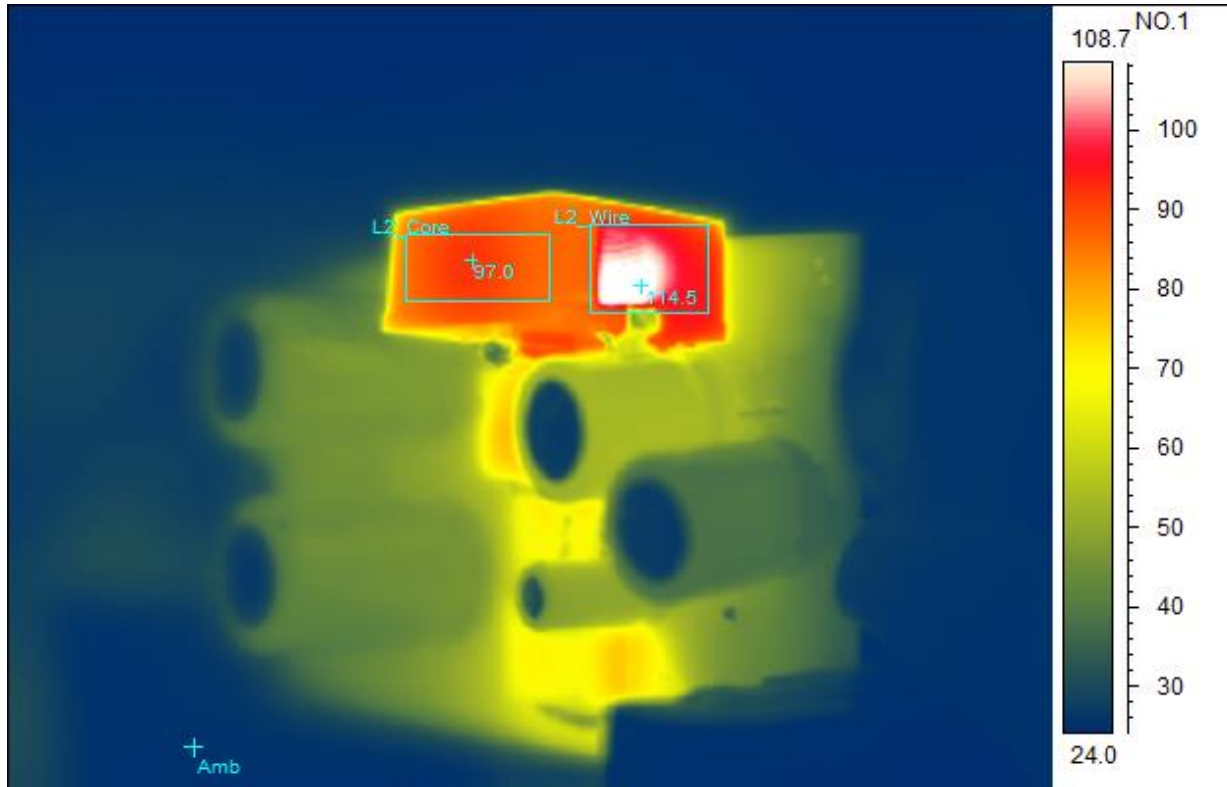

Spot analysis	Value
Amb Temperature	25.3°C
Area analysis	Value
L2_WireMax	114.5°C
L2_CoreMax	97.0°C

**$V_{in}=120V_{AC}/60Hz$**

**Bottom view**

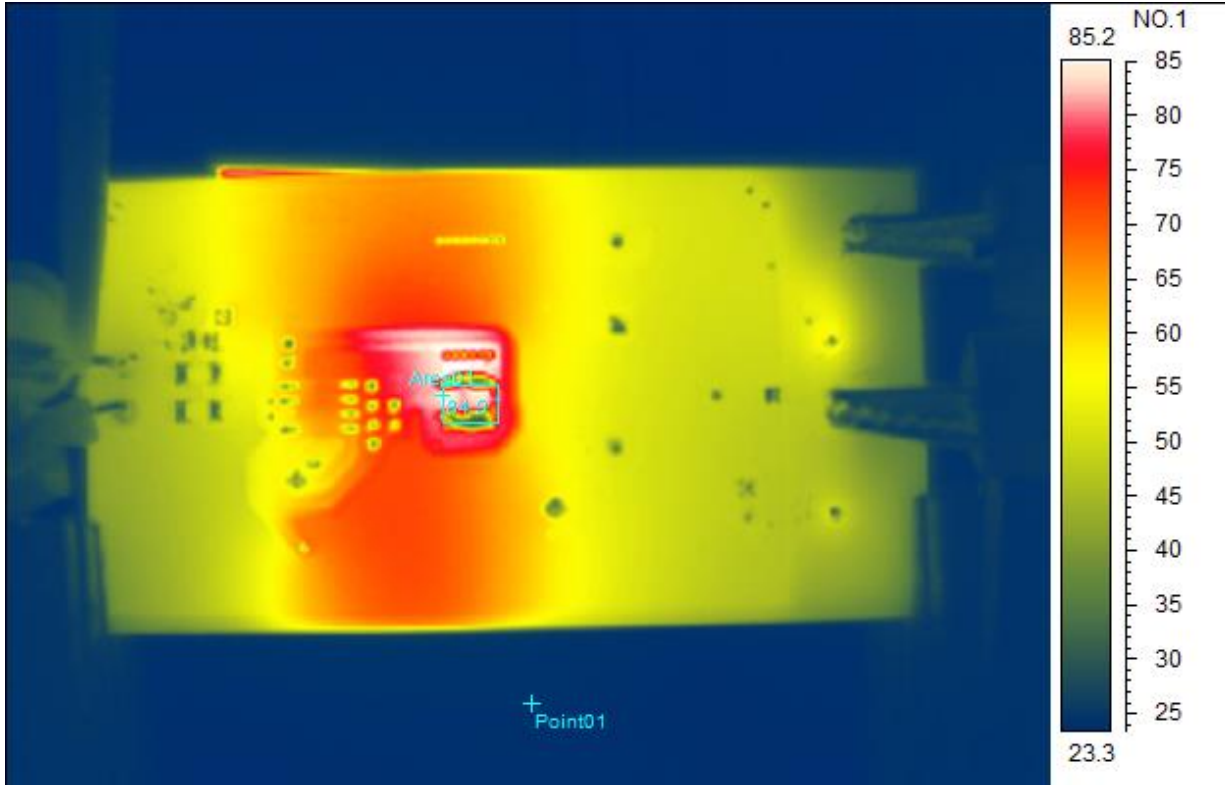


Spot analysis	Value
Point01Temperature	24.2°C
Area analysis	Value
Area01Max	84.9°C




## 4 Startup Waveforms

The output voltages at startup are shown in the images below. CH1:  $V_{out}$ , CH2:  $V_{in}$ .

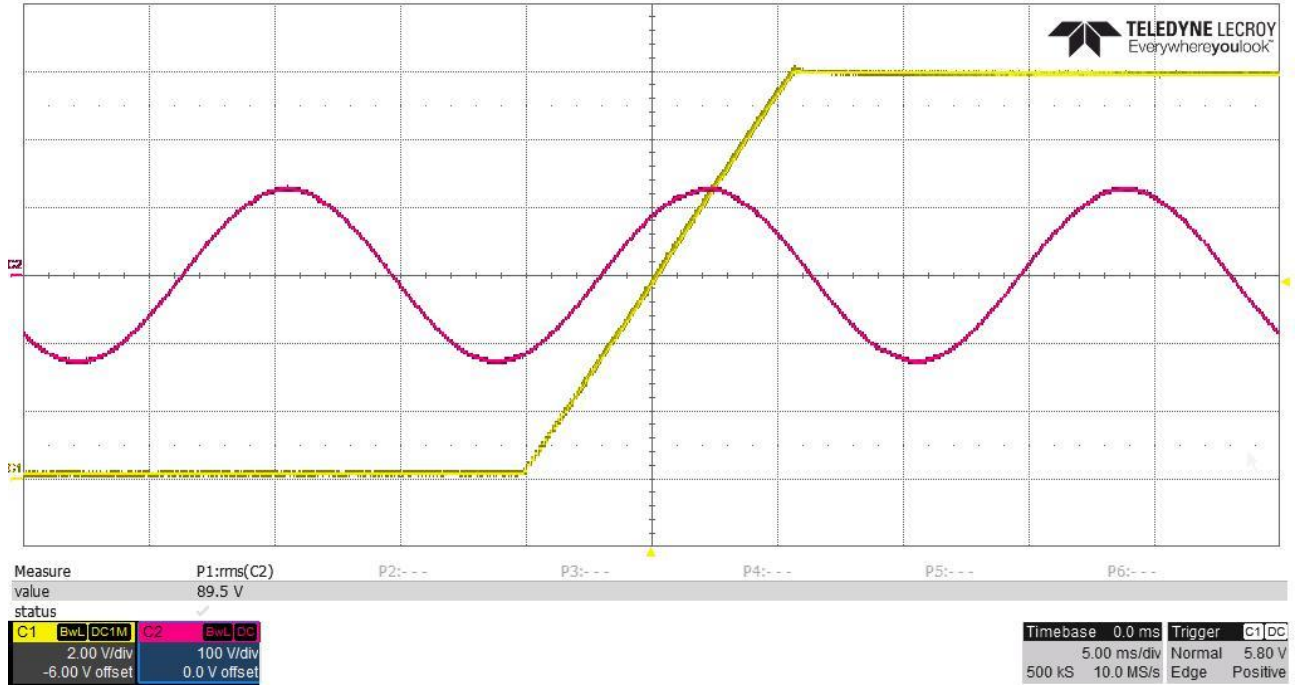
### 4.1 Start Up @ 90V<sub>AC</sub>/60Hz: 12V no load.



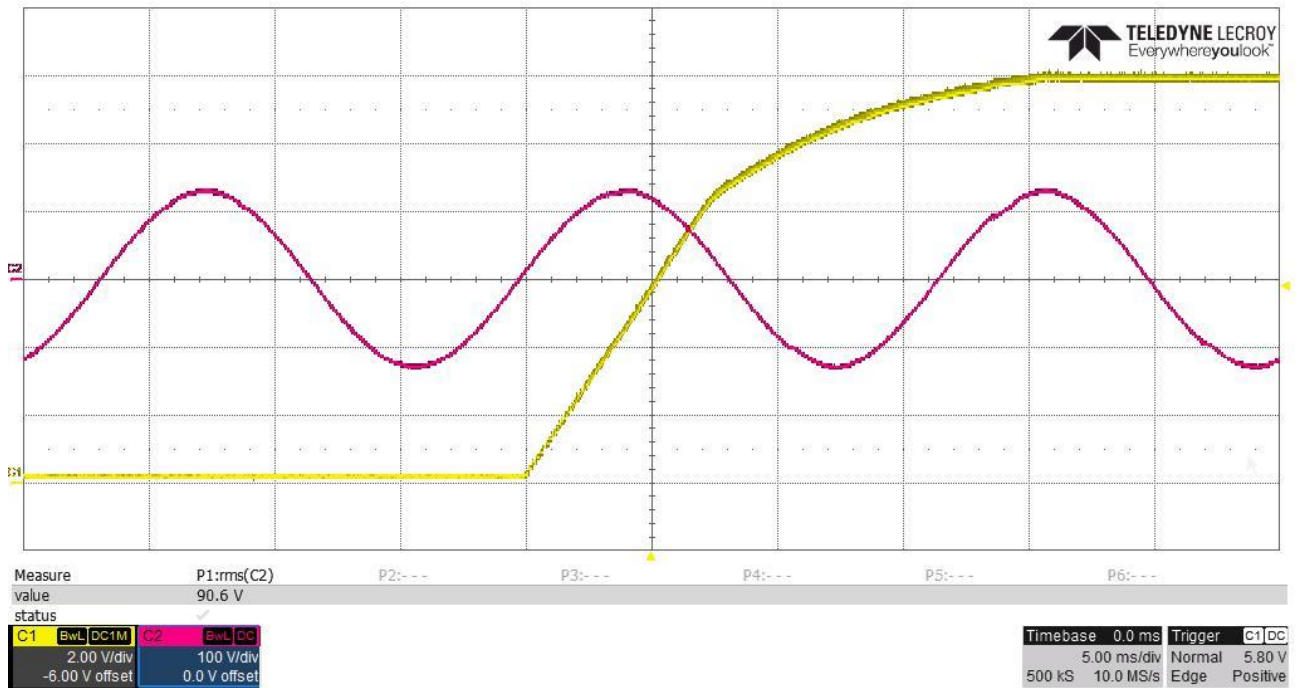
### 4.2 Start Up @ 90V<sub>AC</sub>/60Hz: 12V/8.8Ω load (CR mode).


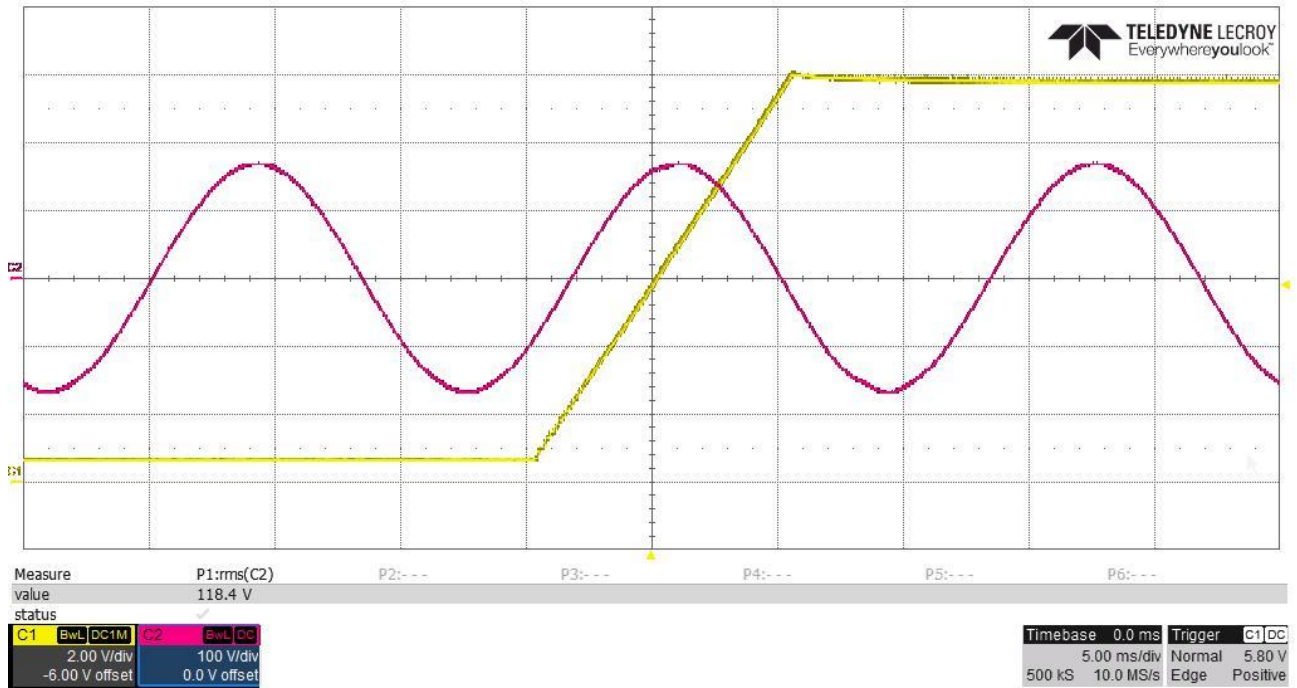
### 4.3 Start Up @ 120V<sub>AC</sub>/60Hz: 12V no load.



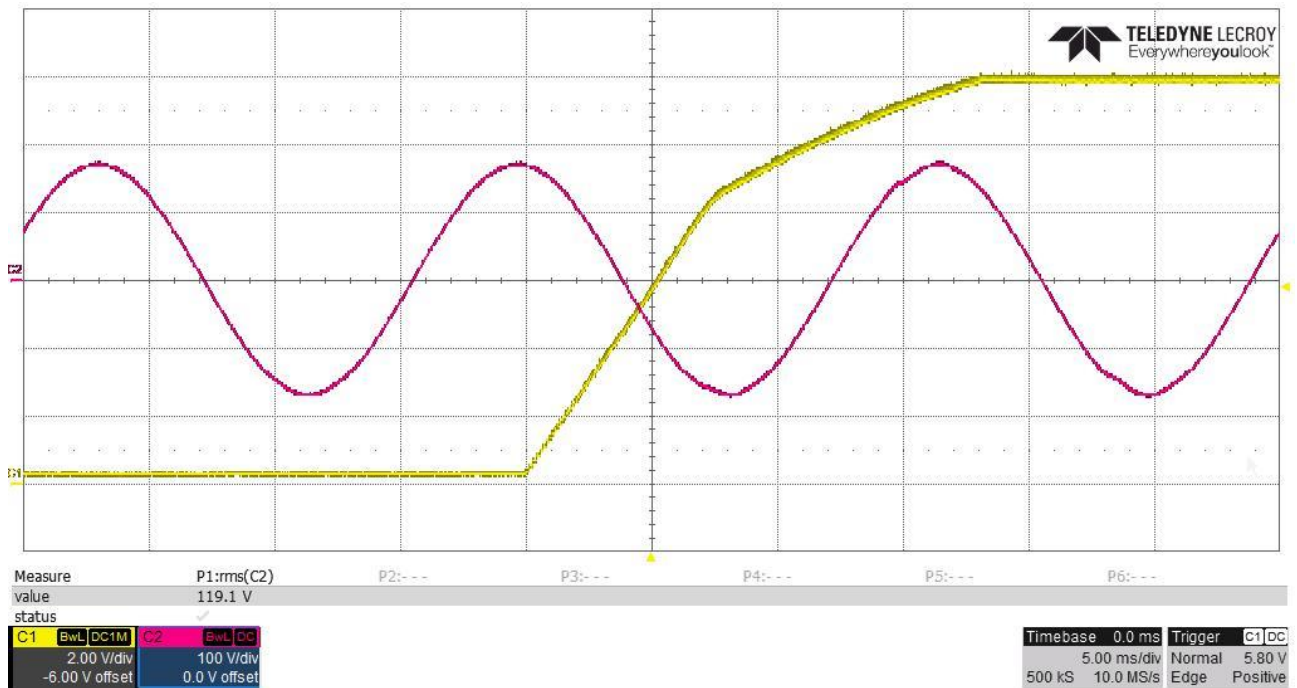
### 4.4 Start Up @ 120V<sub>AC</sub>/60Hz: 12V/8.8Ω load (CR mode).



## 4.5 Start Up @ 150V<sub>AC</sub>/60Hz: 12V no load.


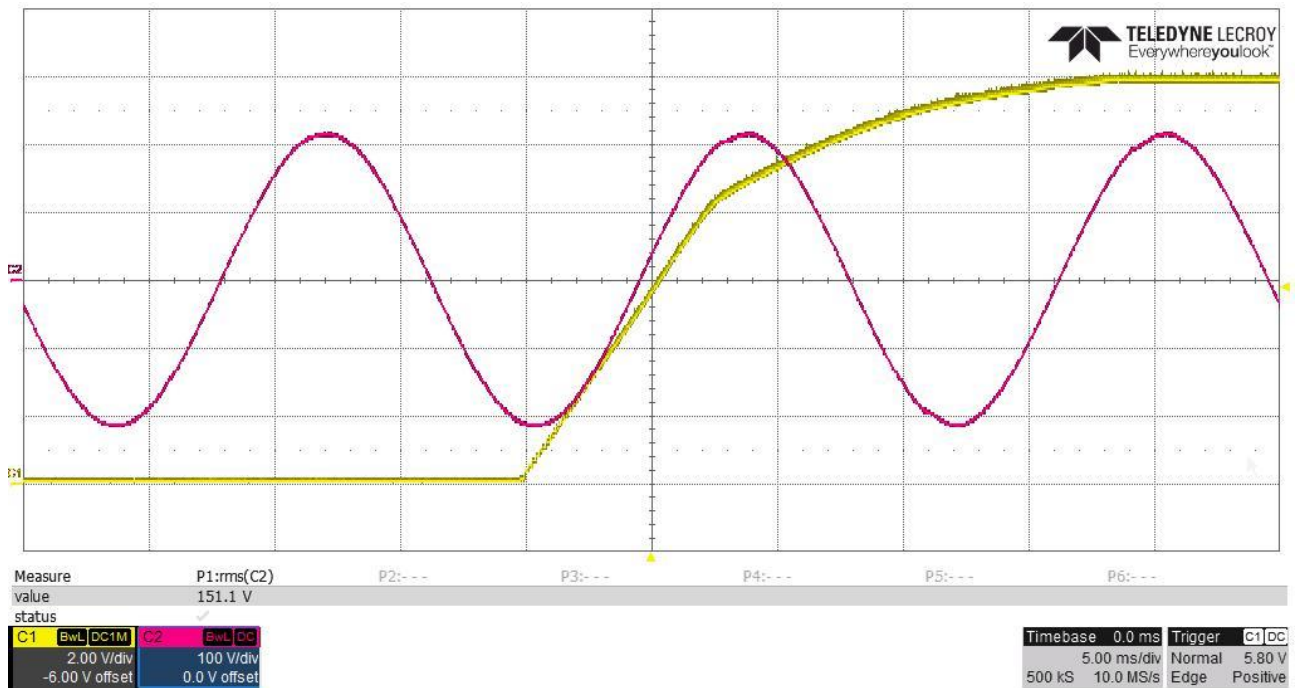
## 4.6 Start Up @ 150V<sub>AC</sub>/60Hz: 12V/8.8Ω load (CR mode).




## 5 Output Ripple Voltages


The output ripple voltages are shown in the plots below:

### 5.1 100V<sub>AC</sub>/60Hz

#### 5.1.1 No load

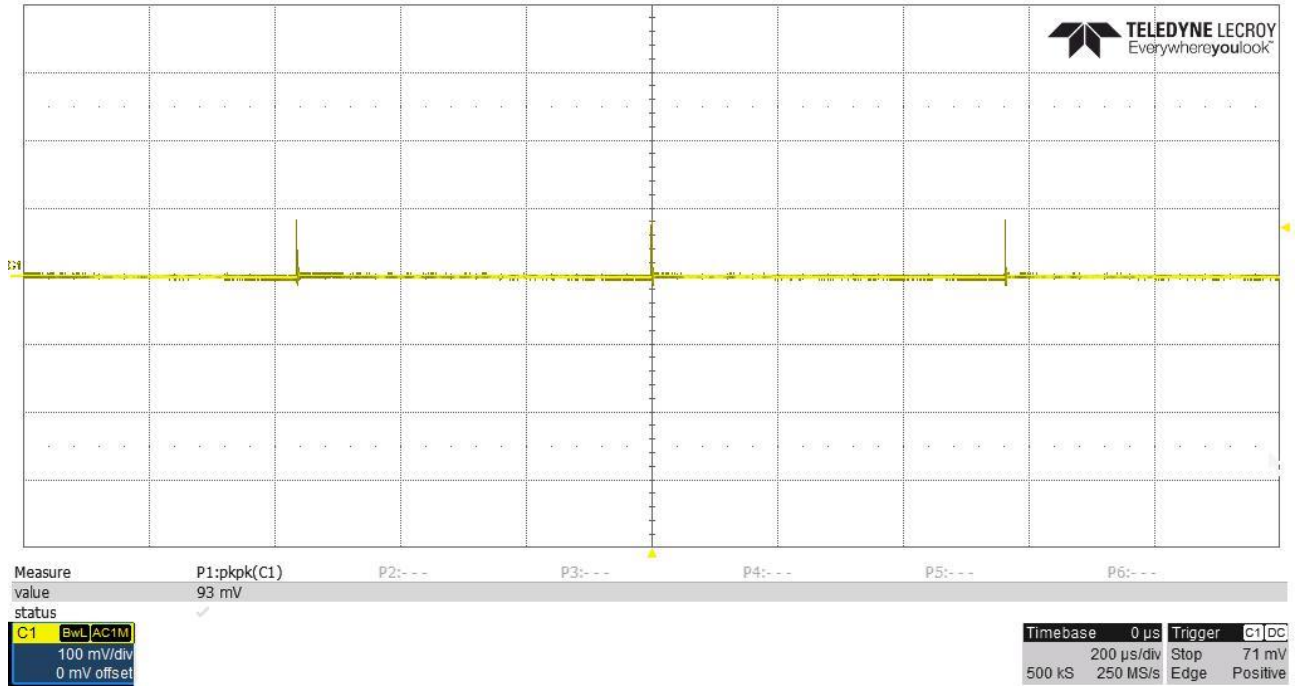


#### 5.1.2 12V/8.8Ω load (CR mode)

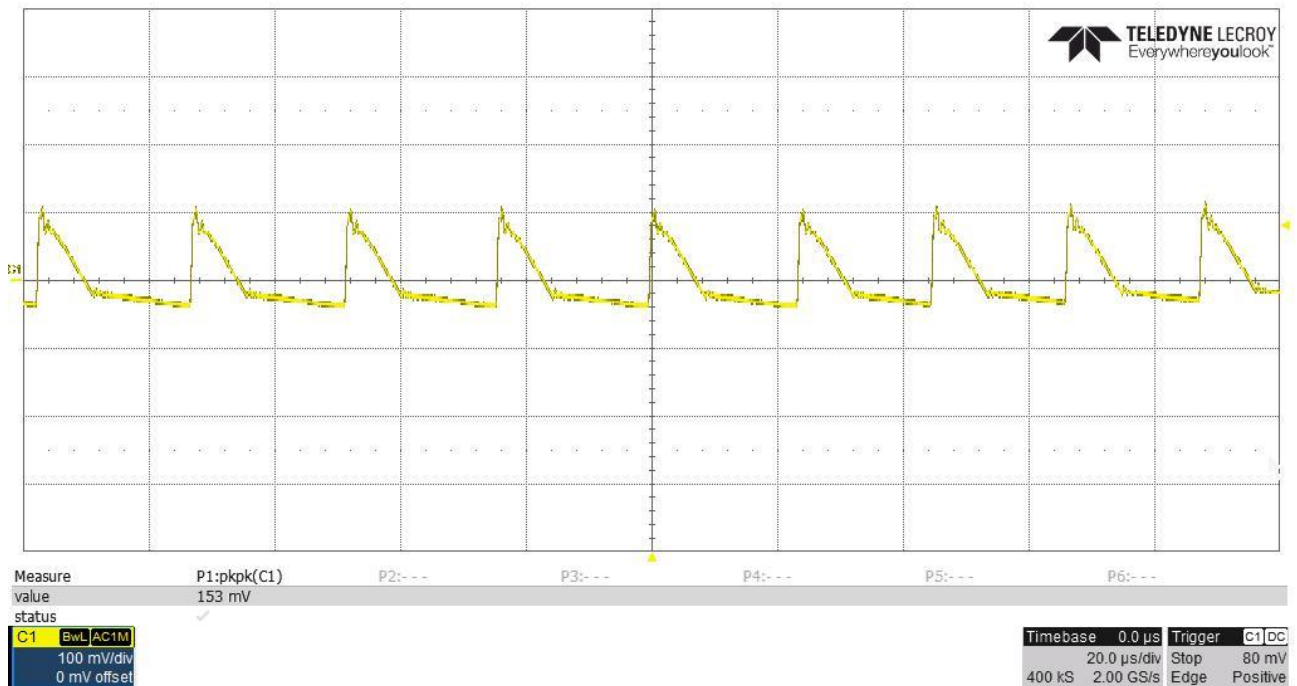




## 5.2 120V<sub>AC</sub>/60Hz

### 5.2.1 No load

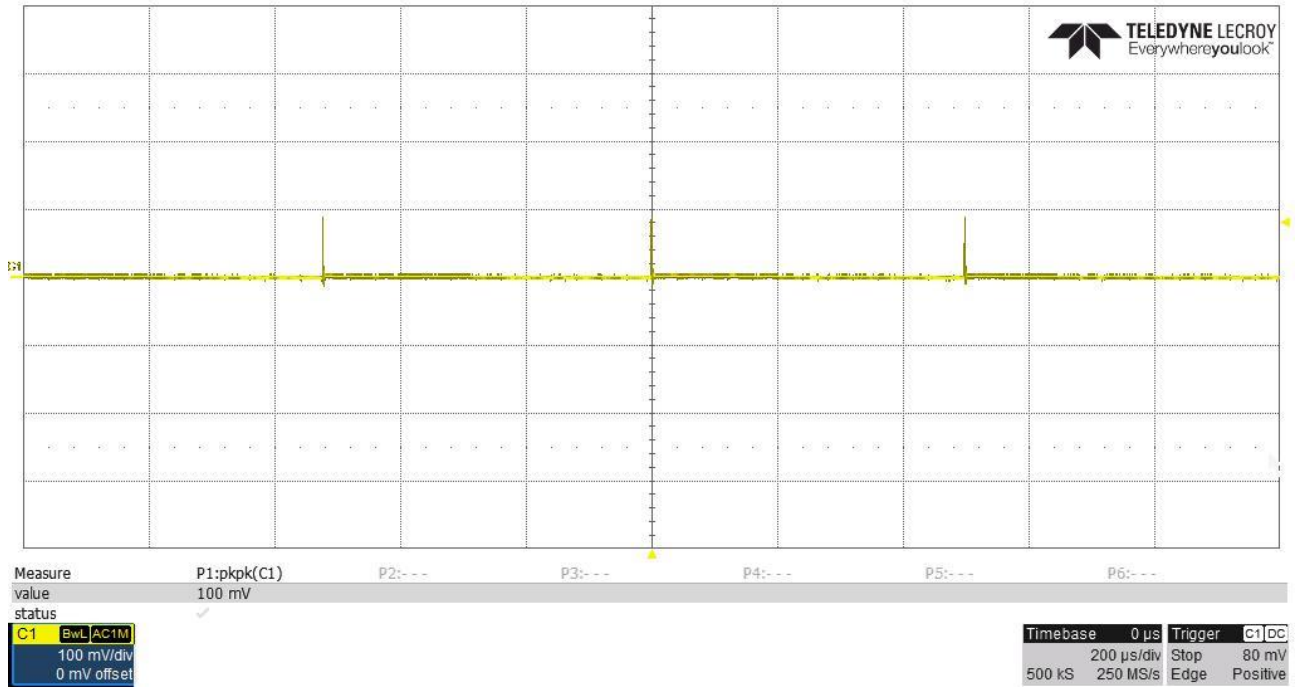

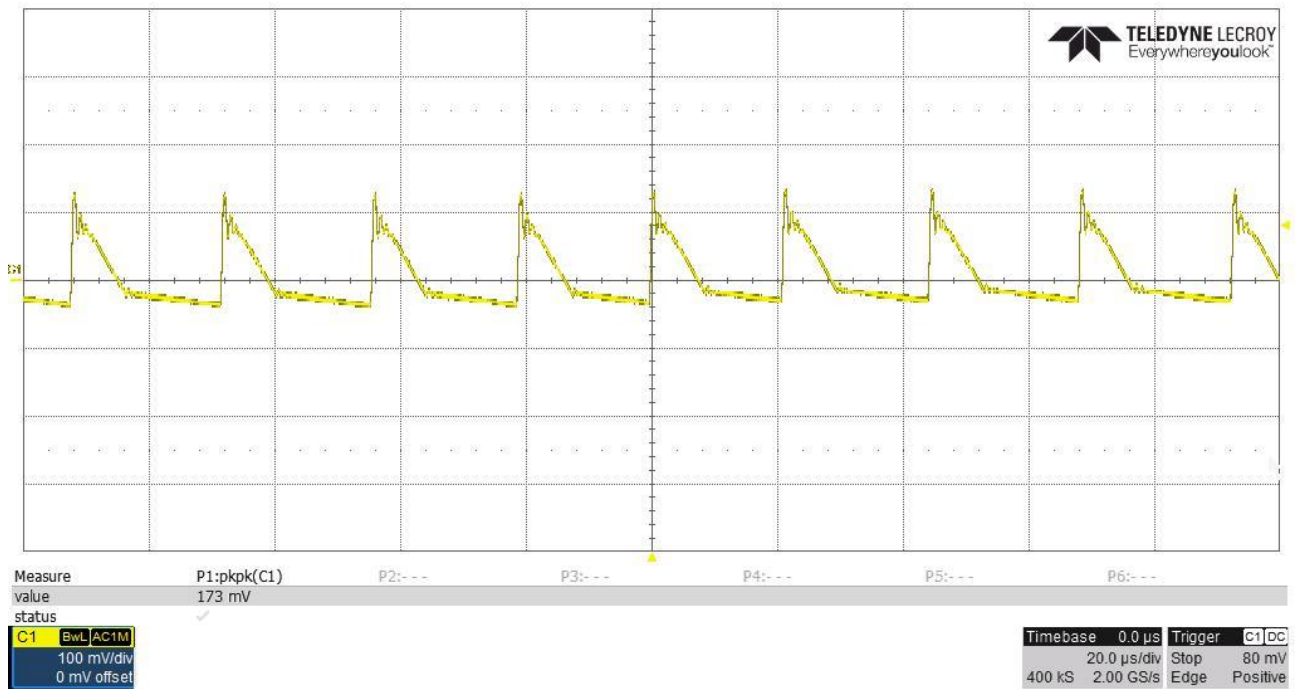
### 5.2.2 12V/8.8 $\Omega$ load (CR mode)




## 5.3 150V<sub>AC</sub>/60Hz

### 5.3.1 No load

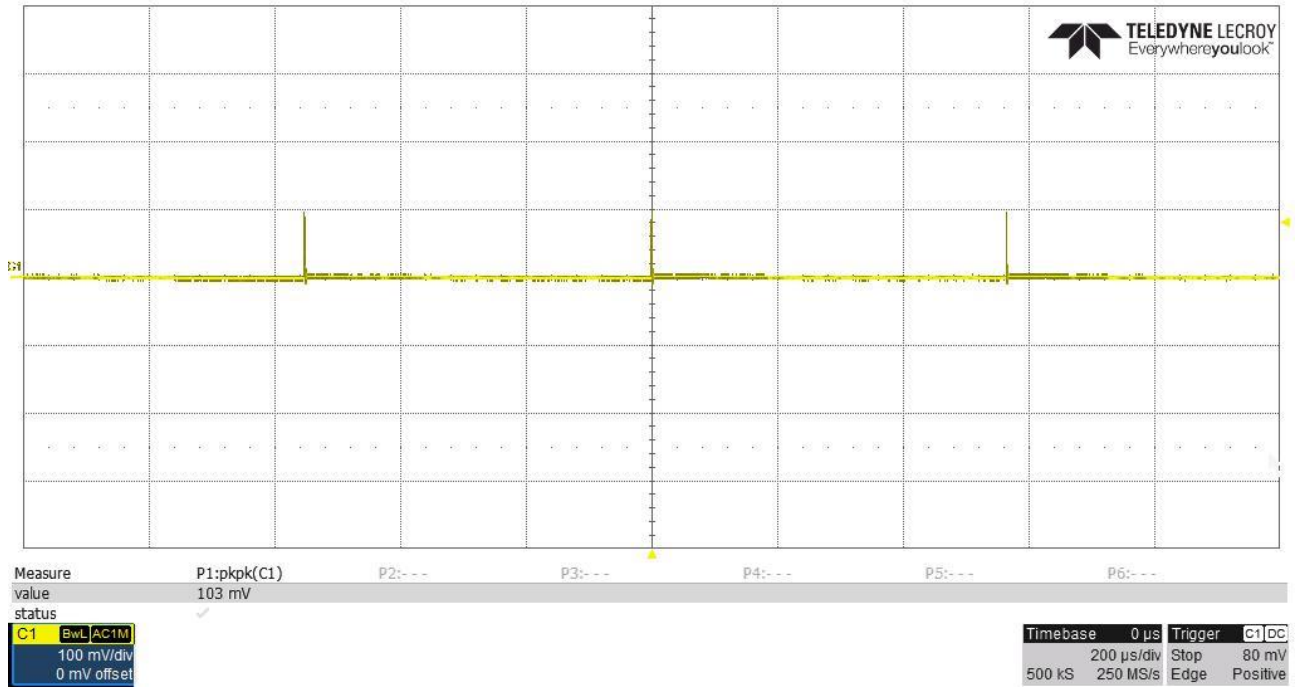


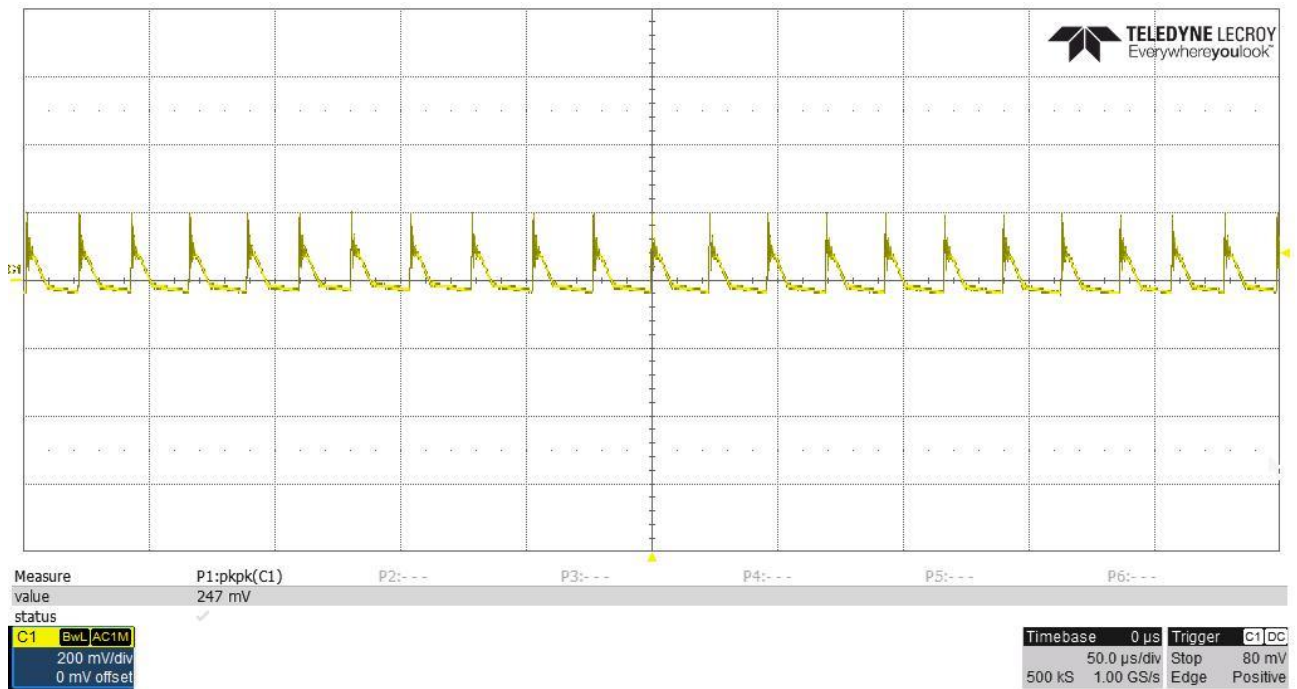
### 5.3.2 12V/8.8 $\Omega$ load (CR mode)




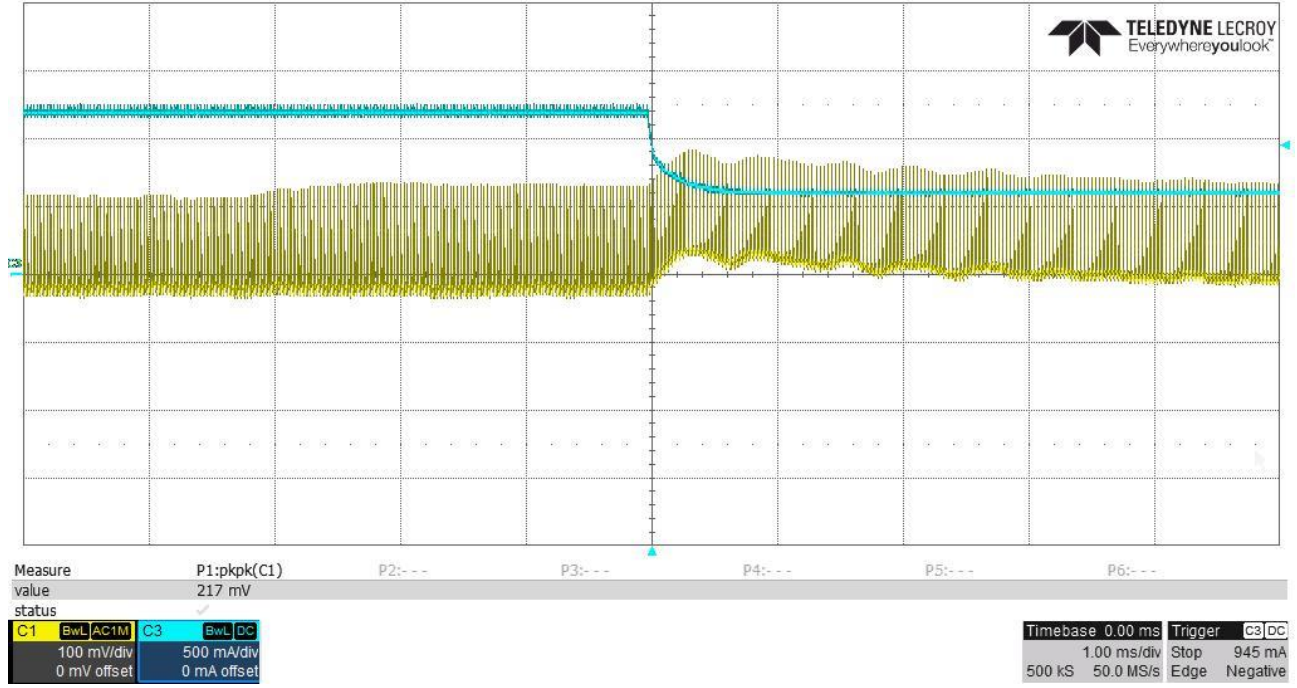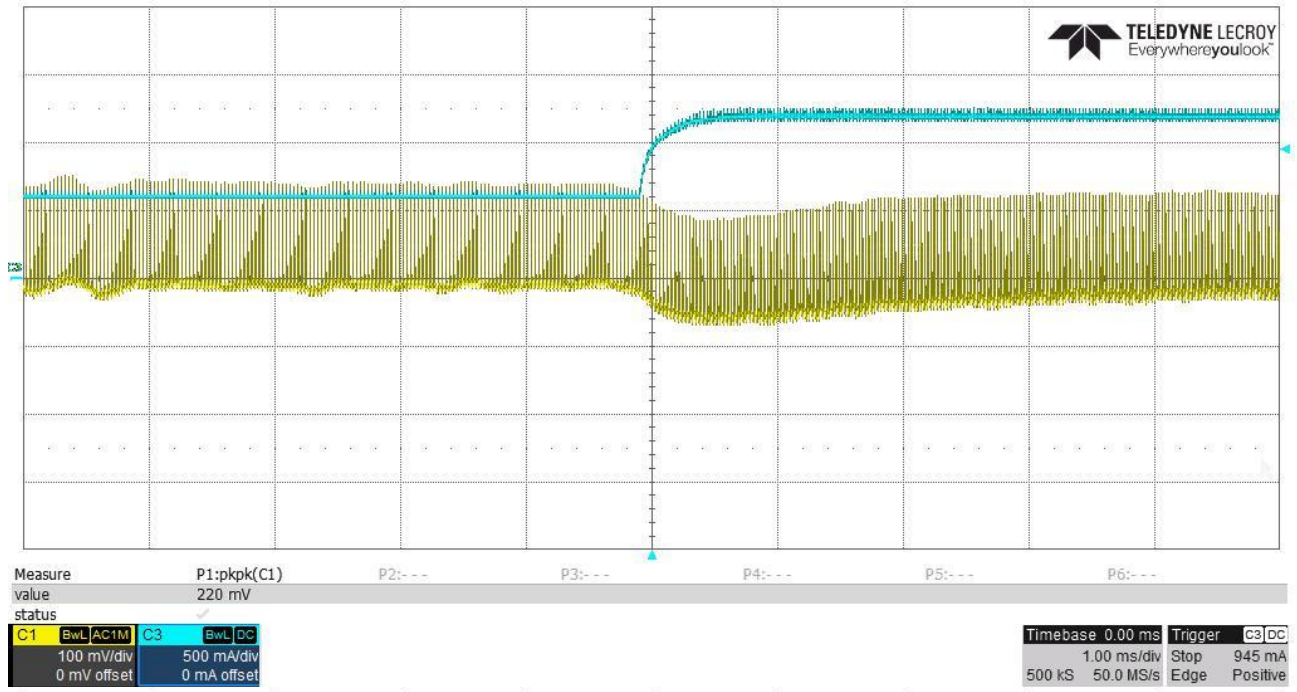
## 6 Load Transient


The image below shows 12V<sub>out</sub> voltage response to a **0.6A to 1.2A** load transient at 120V<sub>AC</sub>/60Hz input.




## 7 Switching Waveforms

The images below show key switching waveforms of PMP20495RevA.

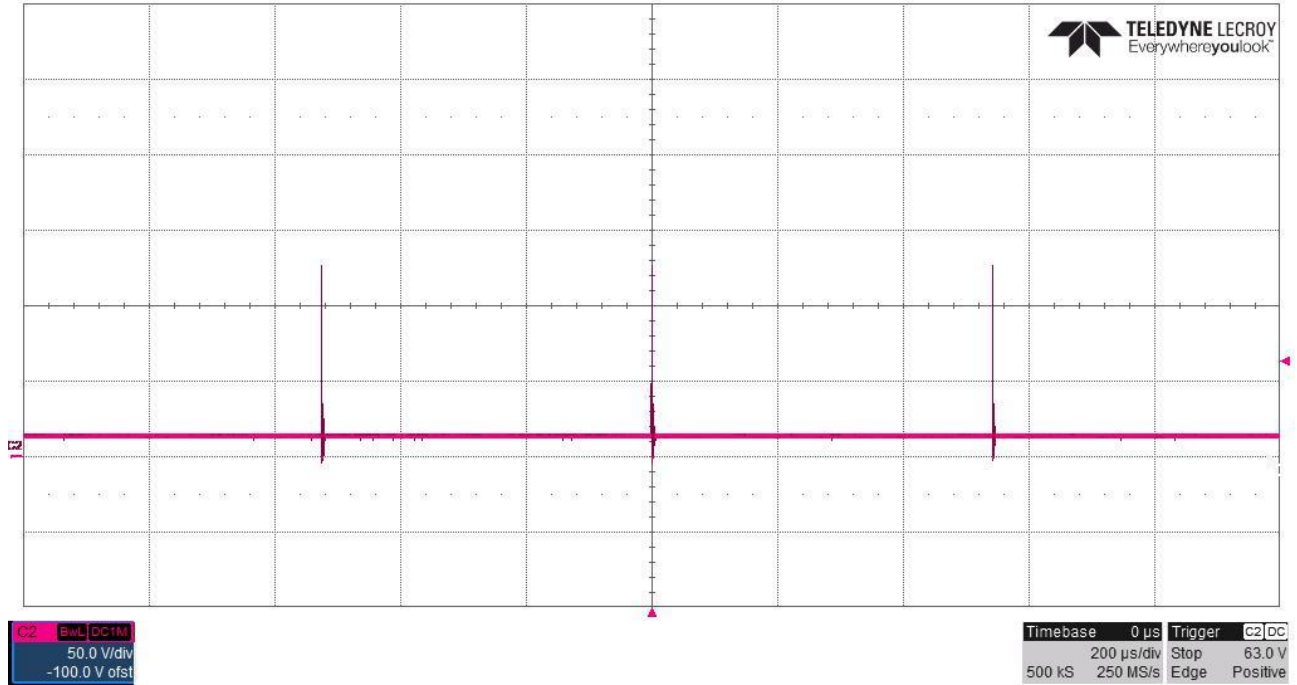
### 7.1 Diode D4 @ 90V<sub>AC</sub>/60Hz, No load



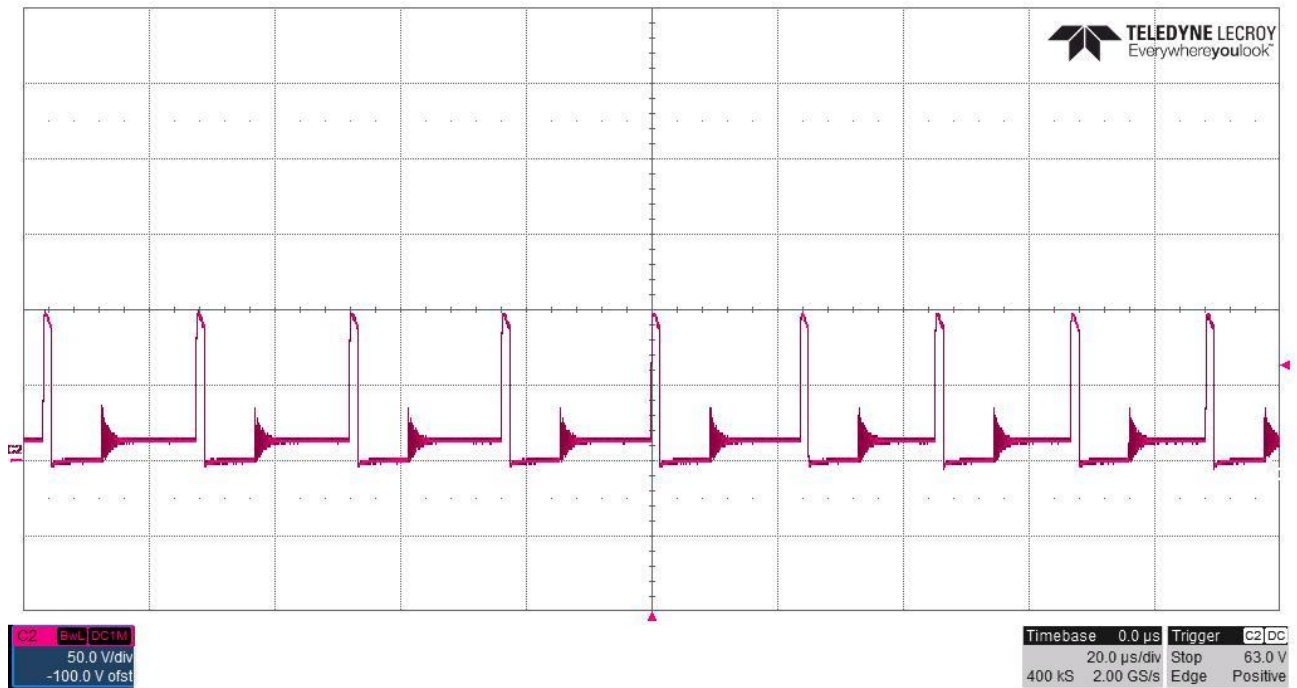
### 7.2 Diode D4 @ 90V<sub>AC</sub>/60Hz, 12V/8.8Ω load



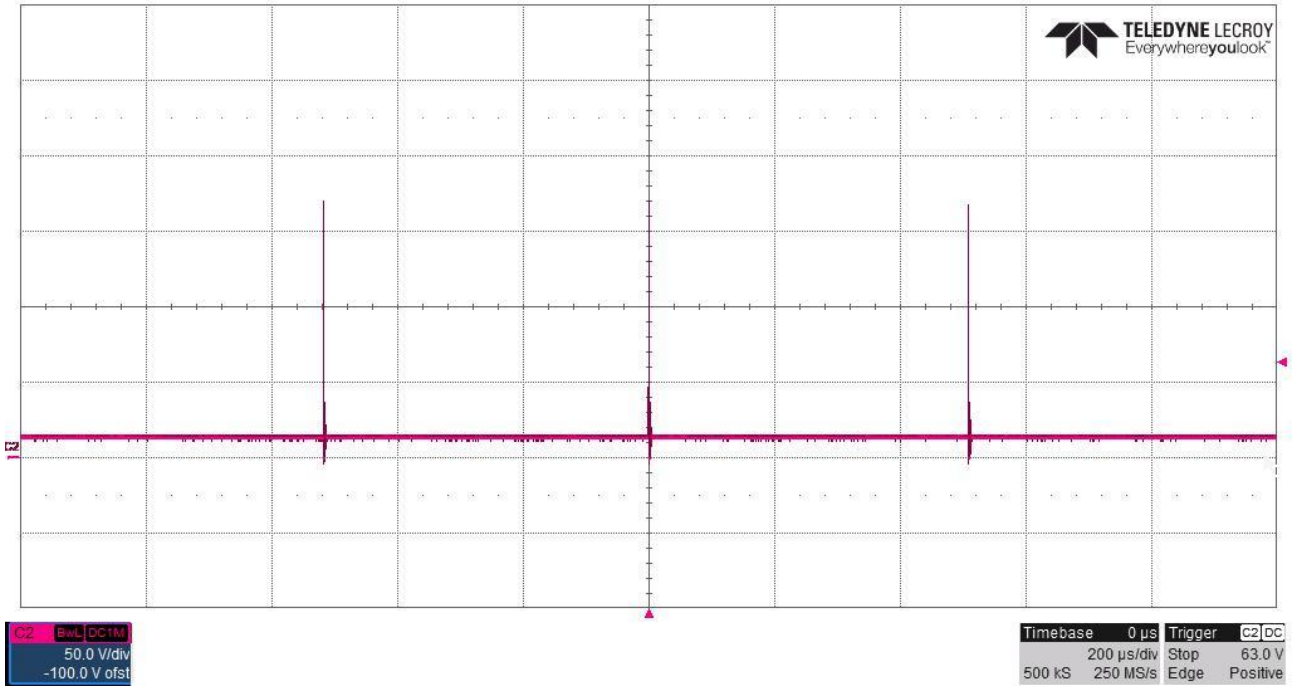
### 7.3 Diode D4 @ 120V<sub>AC</sub>/60Hz, No load



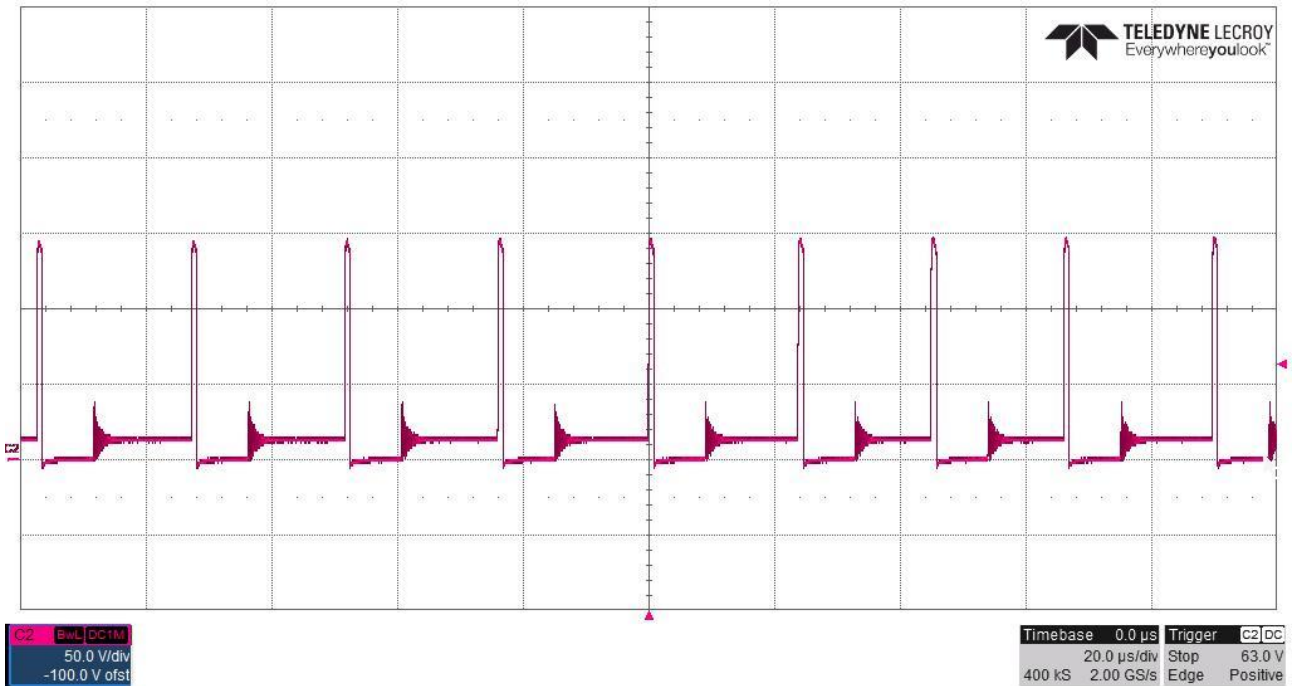
### 7.4 Diode D4 @ 120V<sub>AC</sub>/60Hz, 12V/8.8 $\Omega$ load


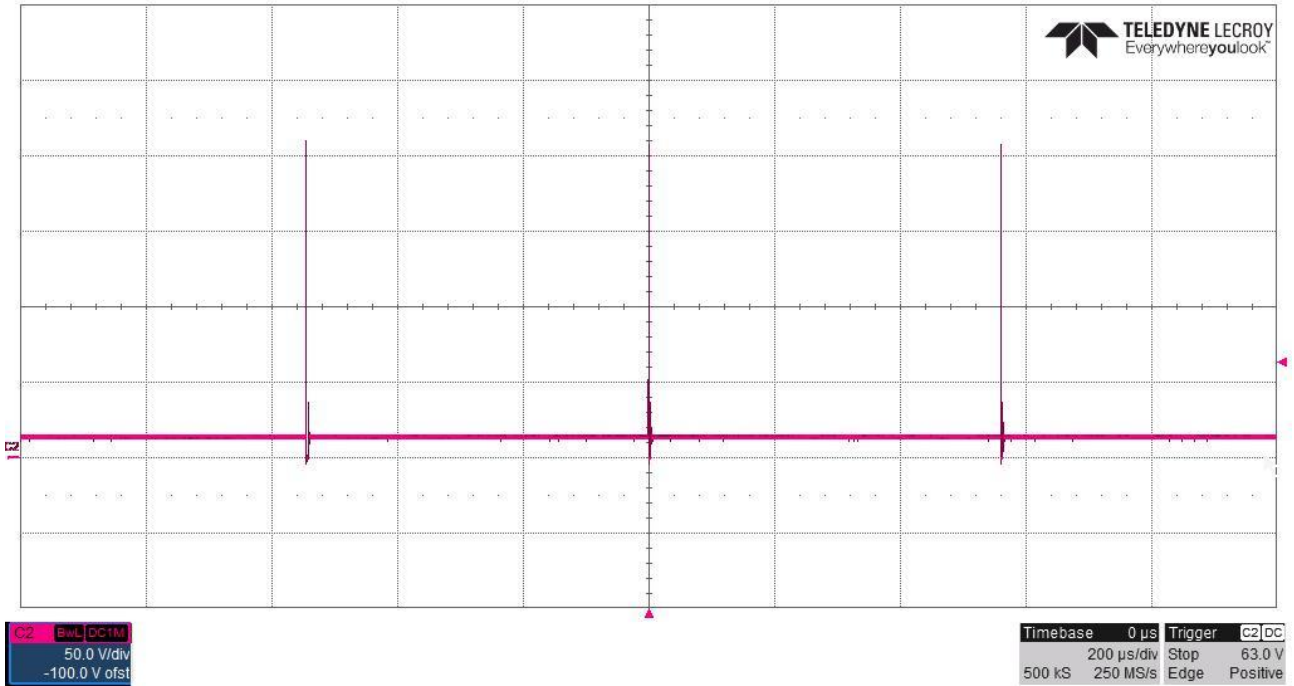
## 7.5 Diode D4 @ 150V<sub>AC</sub>/60Hz, No load


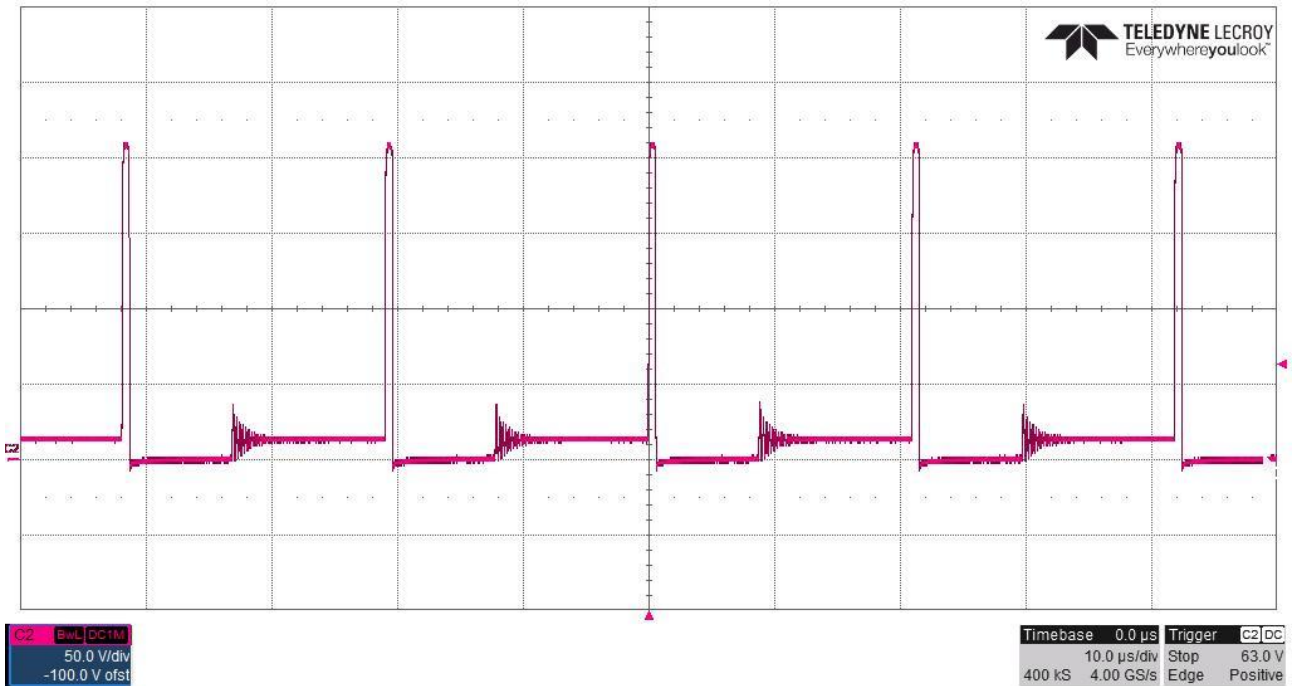
## 7.6 Diode D4 @ 150V<sub>AC</sub>/60Hz, 12V/8.8Ω load



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated